
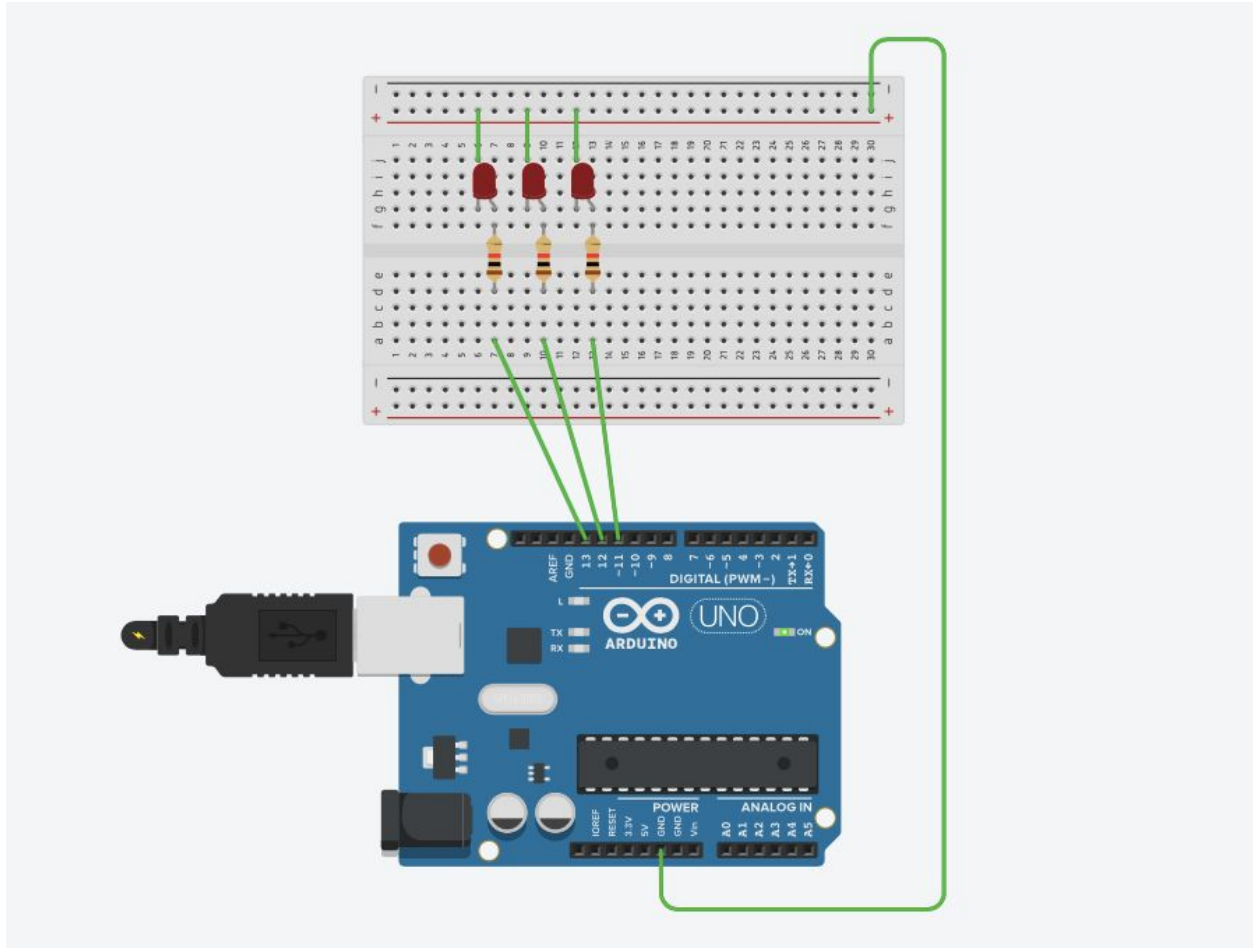


## CIRCUIT & BLOCK CODE

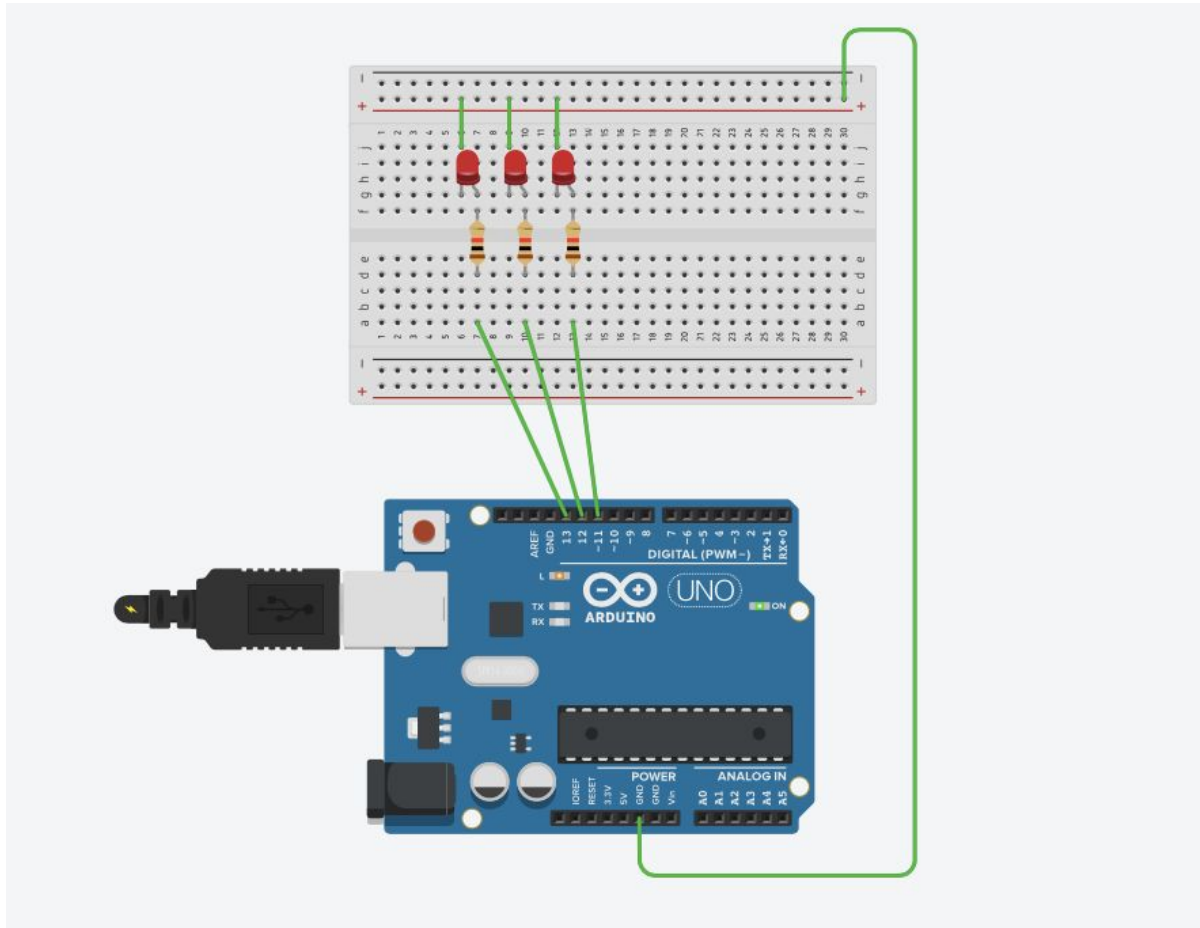

Circuit when LEDs are not glowing



Circuit when LEDs are Glowing



BLOCK CODE